

07/06/21

Voltage Multiplier Circuits :-

20V

IIP

OIP

$$40V = 20V \times 2 \Rightarrow \text{Voltage Doubler}$$

$$60V = 20V \times 3 \Rightarrow \text{Voltage Tripler}$$



$$80V = 20V \times 4 \Rightarrow \text{Voltage Quadrupler}$$

Voltage Doubler

① Half-wave Voltage Doubler

② Full wave Voltage Doubler



① Half Wave Voltage Doubler

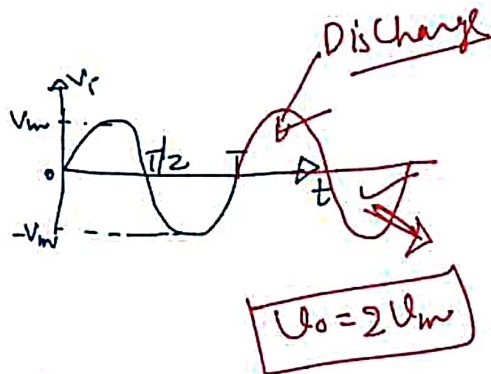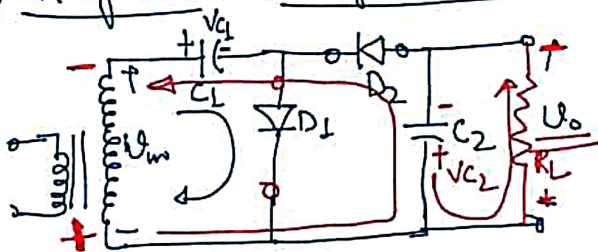

① $0 \rightarrow T/2$ $D_1 \rightarrow \text{ON}$, $D_2 \rightarrow \text{OFF}$
 $V_m - V_{C1} = 0 \Rightarrow V_{C1} = V_m$

② $T/2 \rightarrow T$ $D_1 \rightarrow \text{OFF}$, $D_2 \rightarrow \text{ON}$
 $V_m - V_{C2} + V_{C1} = 0 \Rightarrow V_{C2} = V_m + V_{C1} = V_m + V_m = 2V_m$
 $V_o = V_{C2} = 2V_m = 2V_i$

② Full Wave Voltage Doubler

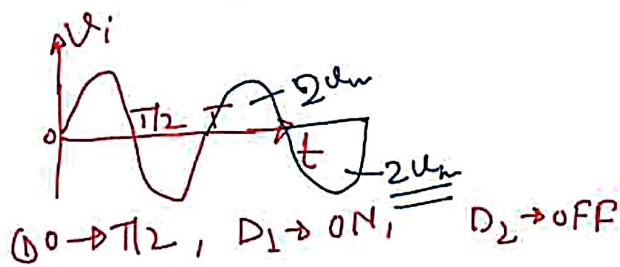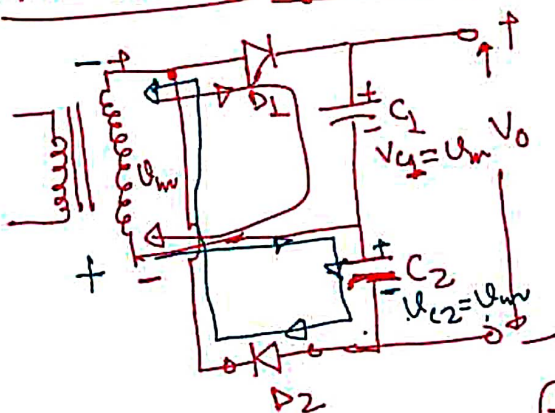

① $0 \rightarrow T/2$, $D_1 \rightarrow \text{ON}$, $D_2 \rightarrow \text{OFF}$

$$V_m - V_{C1} = 0$$

$$V_{C1} = V_m$$

② $T/2 \rightarrow T$, $D_1 \rightarrow \text{OFF}$, $D_2 \rightarrow \text{ON}$


$$V_m - V_{C2} = 0 \Rightarrow V_{C2} = V_m$$

$$V_o = V_{C1} + V_{C2} = V_m + V_m = 2V_m = 2V_i$$

$$V_0 = V_{C1} + V_{C2} = V_m + V_m = 2V_m = 2V_r$$

$V_0 = 2V_r$

Voltage Tripler and Quadrupler

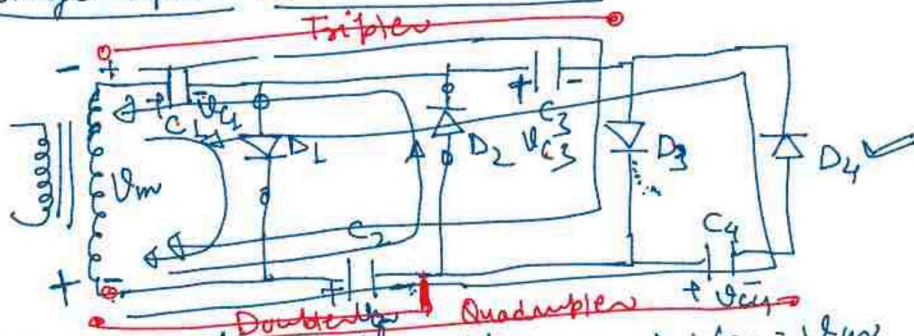

① 1st Half cycle $\rightarrow V_m - V_{C1} = 0 \Rightarrow V_{C1} = V_m$

② 2nd Half cycle $\rightarrow V_m - V_{C2} + V_m = 0 \Rightarrow V_{C2} = 2V_m$

③ 3rd Half cycle $\rightarrow V_m - V_{C1} - V_{C3} + V_{C2} = 0$

$$V_{C3} = V_m + V_{C2} - V_{C1} = V_m + 2V_m - V_m = 2V_m$$

4th Half cycle


$$V_m - V_{C2} - V_{C4} + V_{C3} + V_{C1} = 0$$

$$V_{C4} = V_m - V_{C2} + V_{C3} + V_{C1}$$

$$= V_m - 2V_m + 2V_m + V_m = 2V_m$$

$$V_{C4} = 2V_m$$


Voltage Regulator

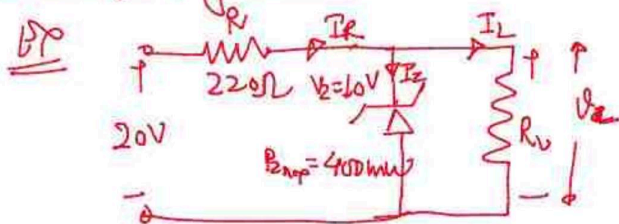

① Determine, I_L, V_L, I_Z, I_R
If $R_L = 180\Omega$

② if $R_L = 470\Omega$

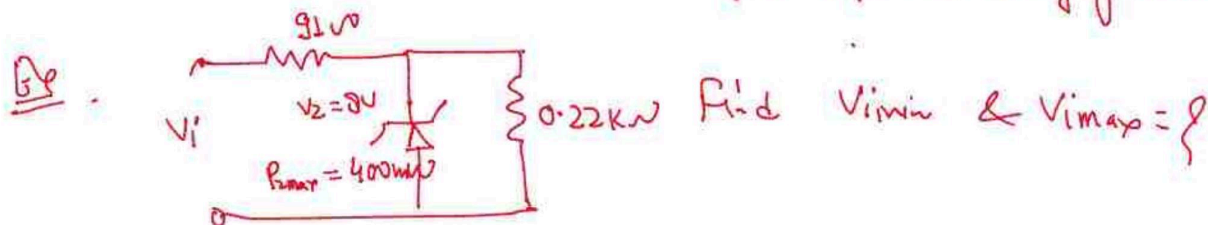③ Find $R_{L\text{maximum}}$ and $R_{L\text{min}}$ for proper working of Zener.




Find V_{min} & $V_{\text{max}} = ?$


08/06/21.


Special Diodes

1. LED (Light Emitting Diode)

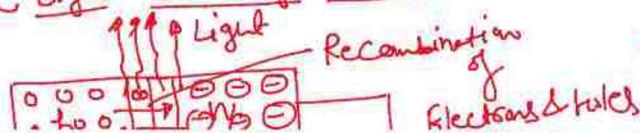

LASER

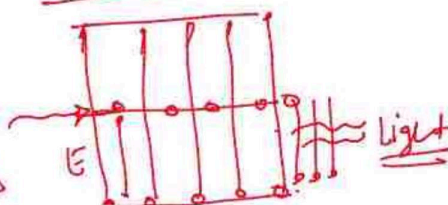

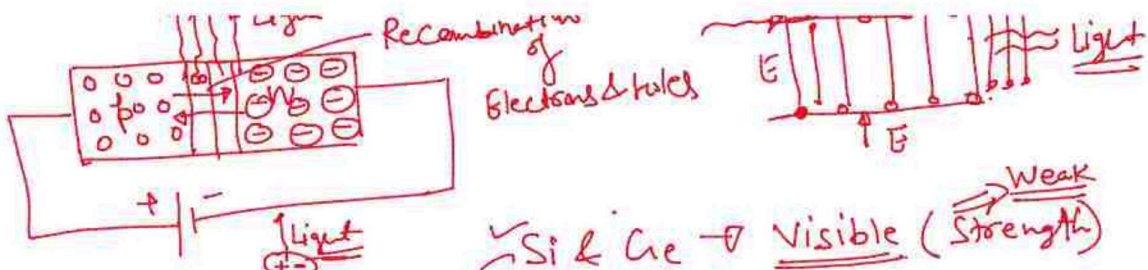


Wavelength

Light Recombination

Si & Ge → Visible (Weak Strength) → Weak
 GaAs → Invisible (infrared) → High Intensity → Weak

$\frac{GaAsP}{GaP}$

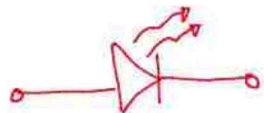$\left\{ \begin{array}{l} GaN \\ GaP \\ GaAsP \end{array} \right\} \rightarrow \text{Visible, good strength}$




LED Symbol

Forward Biased.



- Application :
- ① Traffic Signal
 - ② Display Boars.
 - ③ Light

Seven Segment Display

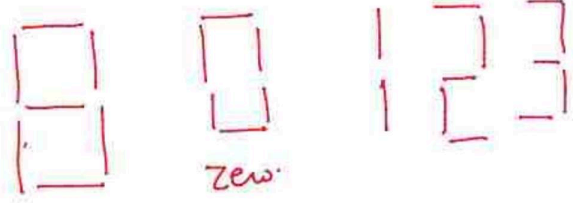


LED → LCD

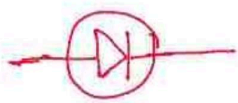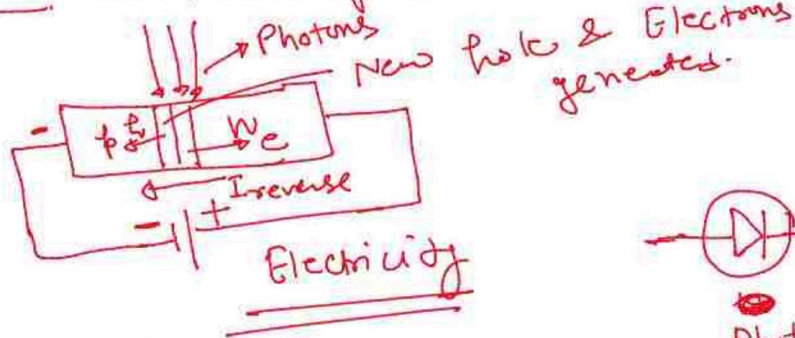2. Photodiodes → Reverse of LED → Recombination




Photodiodes

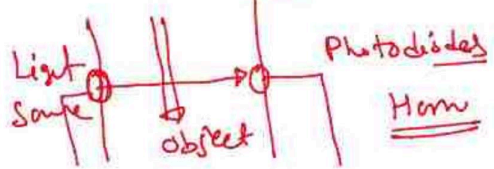- ① Solar Light
- ② Counting of object
- ③ ~~Security Systems~~



② Counting of object

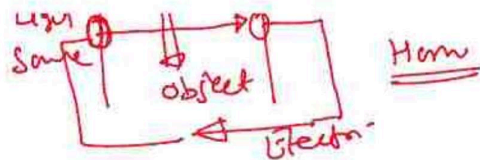


③ VARACTOR (VARICAP) DIODES

Variable Capacitance

$$C_T = \frac{\epsilon A}{W_d}$$



$$C_T = \frac{K}{(V_T + V_R)^n}$$

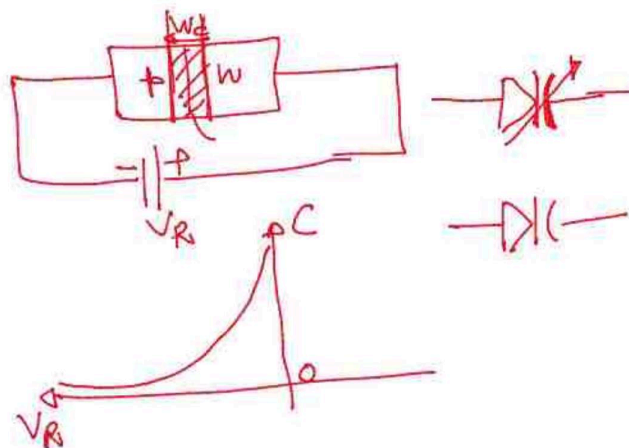

Application ① Tuning of oscillator. \rightarrow Communication.




$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$f \propto \frac{1}{\sqrt{C}}$$

④ Tunnel Diodes

Normal Diodes



Doping Concentration is less

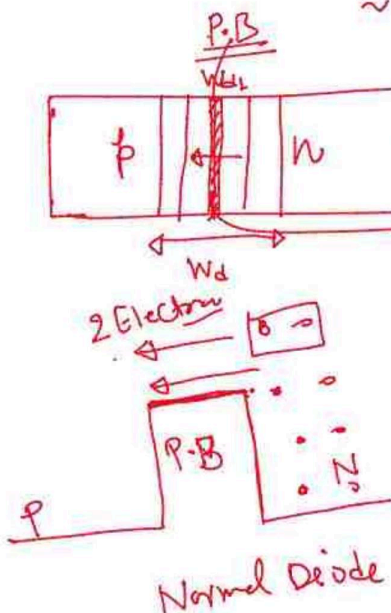

Tunnel Diodes



Doping Concentration is very High

Low times

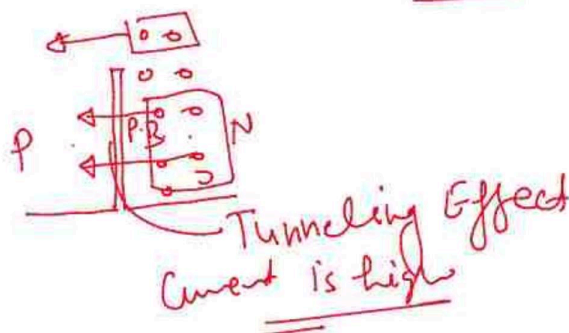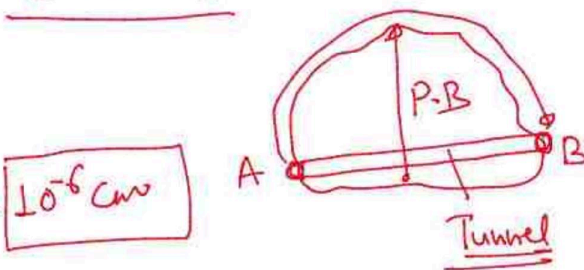


Normal Diode


Current is high

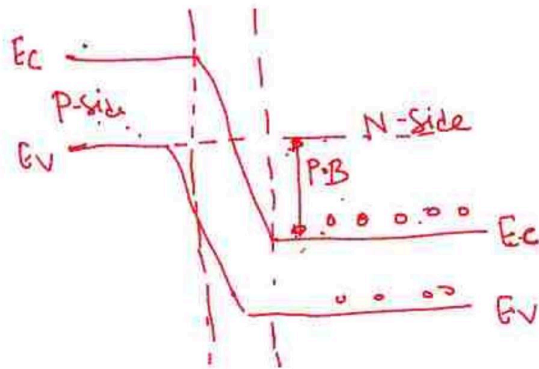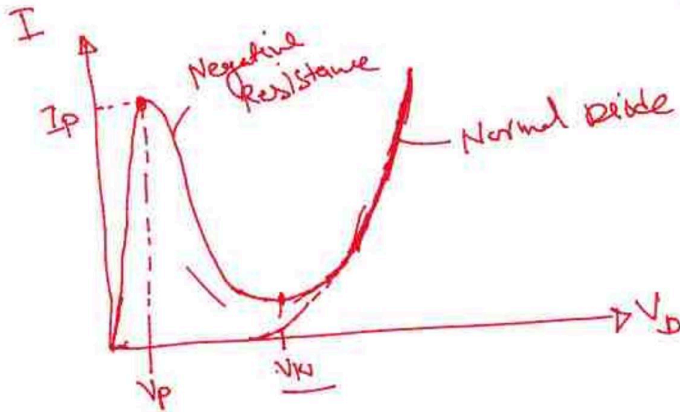


Normal Diode

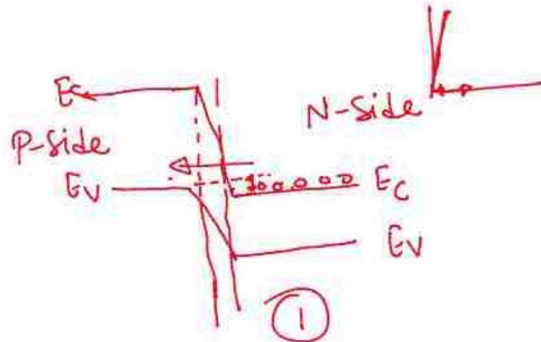

Tunnel Diode

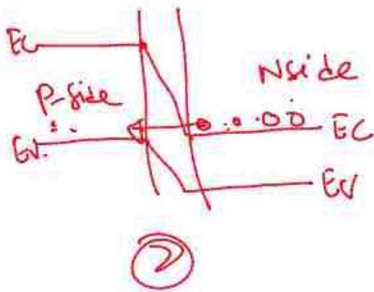

②

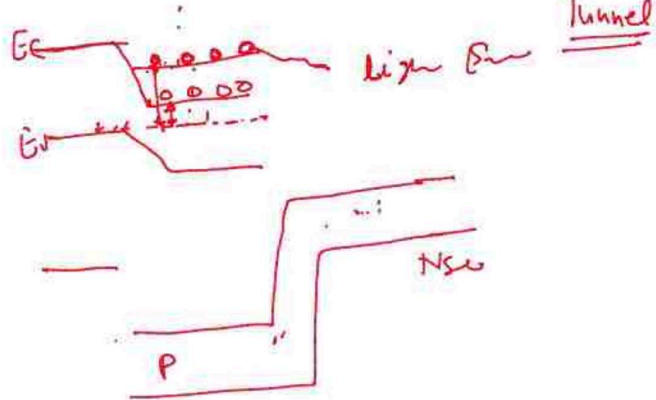

Tunnel

Application ① High Speed Devices (Switching time)

② Microwave device (High freq.)

MHz